

DLD Assignment-3

1. If the waveforms in Fig-1 are applied to an active-Low S-R latch, draw the resulting Q output waveform in relation to the inputs. Assume that Q starts Low.

 


Fig-1

2. Solve problem -1 for the input waveform in Fig-2 applied to an active –High S-R latch.

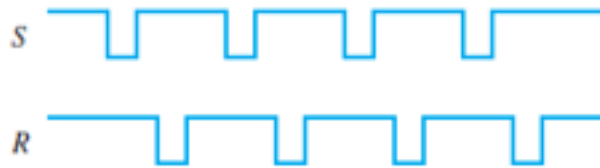


Fig-2

3. Solve problem -1 for the input waveform in Fig-3.



Fig-3

4. For a gated S-R latch, determine the Q and Q' output for the inputs in Fig-4. Show them in proper relation to the enabled input. Assume that A starts LOW.

 


Fig-4

5. Determine the output of the gated D latch for the inputs in Fig-5 and Fig-6.



Fig-5



Fig-6

6. The Q output of an edge-triggered D flip-flop is shown in relation to the clock signal in Fig-7. Determine the input waveform on the D input that is required to produce this output if the flip-flop is a positive edge-triggered type.

 


Fig-7

7. Draw the Q output relative to the clock for D flip-flop with the inputs shown in Fig-8. Assume positive edge-triggered and Q initially LOW.



Fig-8

8. Solve the problem-7 for input in Fig-9 and Fig -10

 


Fig-9

 


Fig-10

9. Determine the Q waveforms relative to the clock if the signal shown in Fig -11 are applied to the input of the J-K flip-flop. Assume that Q initially LOW.

 


Fig-11

10. For negative edge-triggered J-K flip-flop with the input in Fig-12, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.

 


Fig-12

11. For the circuit in Figure -14, complete the timing diagram in Fig-13 by showing the Q output (which is initially LOW). Assume PRE and CLR remain HIGH.

 


Fig-13

 


Fig-14

12. A D flip-flop is connected as shown in Fig-15. Determine the Q output in relation to the clock. What specific function does this device perform?

 


Fig-15

13. For the circuit in Fig-16, develop a timing diagram for eight clock pulses, showing the QA and QB outputs in relation to the clock.

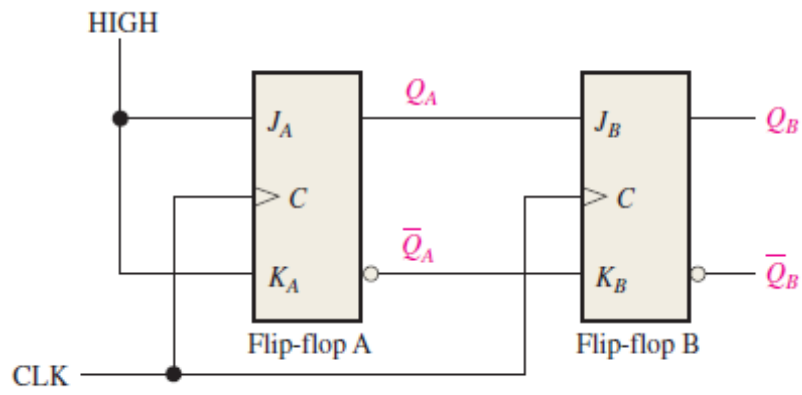


Fig-16