

National University of Computer and Emerging Sciences, Lahore Campus



Course: DLD Lab
Program: BS (Computer Science)
Duration: 50 minutes
Date: 26-03-18
Section: B2 (A)

Course Code: EL227
Semester: Spring 2017
Total Marks: 25
Weight: 25%
Pages: 2

Mid Term Exam

NAME: _____

Roll #: _____

READ THE INSTRUCTIONS CAREFULLY.

1. For your ease, Pin Configurations of all ICs is given in word file named **"ICs Info"** placed in folder at **sandata/xeon/Spring2018/AbdulKhalik/DLDSectionB2**.

2. You will be immediately **disqualified** from the exam if:

i. You are seen talking, whispering, borrowing or looking at someone's Paper.

Problem Statement: Implement the following Boolean functions using 3x8 Decoder and external gates.

$$F1 = y'z + xz$$
$$F2 = xy'z' + x'y + x'y(z + z')$$

a. Draw the truth table for above problem statement.


[3 Point]

A	B	C	F1	F2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	0

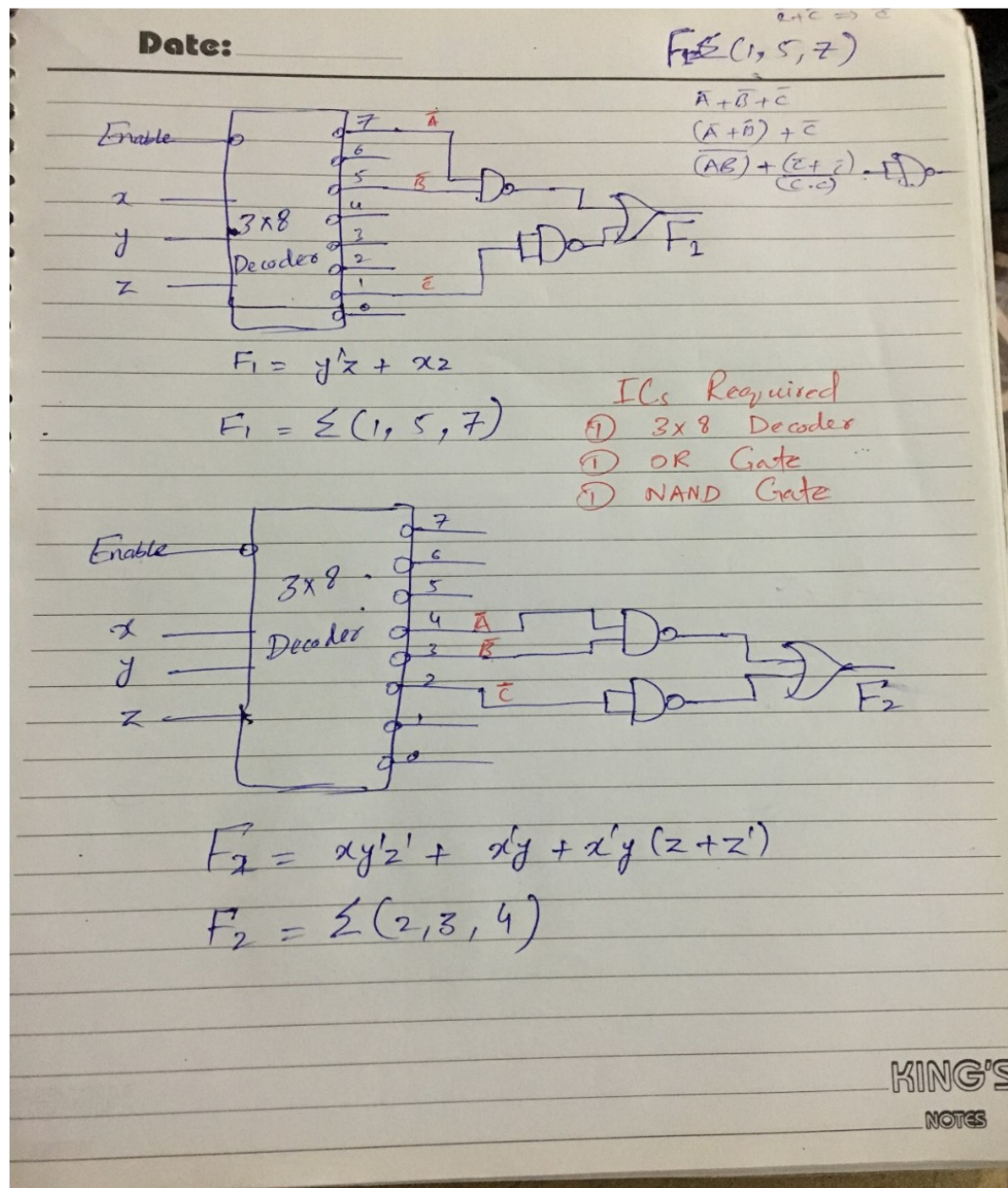b. Draw the complete circuit using 3x8 Decoder and 2-input NAND gates.

[5 Points]

Note: Your circuit should be neat and clean.



- c. Implement the circuit of part (b) on the trainer board and verify the results.
(Note: Use as minimum no. of logic gates as possible)
[15 Points]

