

## National University of Computer and Emerging Sciences, Lahore Campus



Course: DLD Lab  
Program: BS (Computer Science)  
Duration: 60 minutes  
Date: 26-03-18  
Section: B2 (B)

Course Code: EL227  
Semester: Spring 2018  
Total Marks: 25  
Weight: 25%  
Pages: 3

### Mid Term Exam

NAME: \_\_\_\_\_

Roll #: \_\_\_\_\_

#### READ THE INSTRUCTIONS CAREFULLY.

1. For your ease, Pin Configurations of all ICs is given in word file named **"ICs Info"** placed in folder at **sandata/xeon/Spring2018/AbdulKhaliq/DLDSectionB2.**

2. You will be immediately **disqualified** from the exam if:

i. You are seen talking, whispering, borrowing or looking at someone's Paper.

**Problem Statement:** Mr James has invested a huge amount of money into buying and selling land. Before he will buy a certain land, he must get input from three sources. His first source is Jimmy, a famous property dealer. His second source is Meg, a self-made millionaire in this business, and his third source is Carl, his best friend. After several months of receiving advice from all three, he has come to the following conclusions:

- A). Buy if all three say yes.
- B). Buy if the Carl says yes and Meg says no.
- C). Buy if both the Carl and Jimmy says no.
- D). Buy if Jimmy and Meg both say yes even if the Carl says no.
- E). Don't buy otherwise.

a. Draw the truth table for above problem statement.

**[2 Point]**

Jim	Meg	Carl	F1
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1

1	1	1	1
---	---	---	---

- b.** Write Output Equation in Sum of Minterms Form. **[1 Point]**

$$\mathbf{F = x'y'z' + x'y'z + x'yz' + xy'z + xyz' + xyz}$$

- c.** Write Optimized version of above output equation using K-Maps. **[3 Points]**

$$\mathbf{F = x'y' + yz + yz'}$$



- 
- e. Implement the circuit of part (d) on the trainer board and verify the results (Use NAND Gates only). **(Note: Use as minimum no. of logic gates as possible)**  
**[15 Points]**