

DLD Quiz

Instructions:

- i) Try to submit 5 minutes before to avoid any inconvenience. You won't be able to submit after the deadline, ultimately you will lose marks of the quiz
- ii) Only hand written quiz will be accepted.
- iii) In section B, write the complete answer along with the option (a/b/c/d)
- iv) Name & IDs must be mentioned at the top of each page.
- v) Try to provide Truth table or K-Map in section A for each question.
- vi) Quiz is based on 2 sections (A & B)

Time allowed: 45 mins

Marks: 90

Section A

Question 01:

The NAND and the negative-OR symbols represent equivalent operations, but they are functionally different. For the NOR symbol, look for at least one HIGH on the inputs to give a LOW on the output. For the negative-AND, look for two LOWs on the inputs to give a HIGH output. Using these two functional points of view, show that both gates in Figure 3–88 will produce the same output for the given inputs.

 


FIGURE 3–88

Question 02:

The notation A1 A0 represents a two-bit binary number that can have any value (00, 01, 10, 11); for example, when A1 = 1, A0 = 0, the binary number is 10, and so on. Similarly, B1, B0 represent another two-bit binary number. Design a logic circuit, using A1, A0, B1, and B0 inputs, whose output will be Low only when the two binary numbers A1 A0 and B1 B0 are invert.

Question 03:

Use a Karnaugh map to reduce the following expression to a minimum SOP form:

$$A'B' + AB' + C'D' + CD'$$

Question 04:

Design a 4 to 16 line decoder using 2 to 4 line decoders.

Question 05:

Draw parallel adder which can add ($A=00111$ and $B=10101$), determine complete sum by analysis of the logical operation of the circuit.

Question 06:

Show how the following expressions can be implemented as stated using only NOR gates:

$$X = AB[C((DE)' + (AB)') + (BCE)']$$

Question 07:

For a gated S-R latch, determine the Q and Q' outputs for the inputs in Figure 7–73. Show them in proper relation to the enable input. Assume that Q starts LOW.

 


FIGURE 7-73

Question 08:

- a) Determine the Q waveform relative to the clock if the signals shown in Figure 7–83 are applied to the inputs of the J-K flip-flop. Assume that Q is initially LOW.

 


FIGURE 7-83

- b) For a negative edge-triggered J-K flip-flop with the inputs in Figure 7–84, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.

 


FIGURE 7-84

Section B (MCQs)

- 1) What must be used along with synchronous control inputs to trigger a change in the flip flop?
 - a) 0
 - b) 1
 - c) Clock
 - d) Previous output

- 2) What will be the output from a D flip-flop if $D = 1$ and the clock is low?
 - a) No change
 - b) Toggle between 0 and 1
 - c) 0
 - d) 1

- 3) Which of the following gives the correct number of multiplexers required to build a 32×1 multiplexer?
 - a) Two 16×1 mux
 - b) Three 8×1 mux
 - c) Two 8×1 mux
 - d) Three 16×1 mux

- 4) Which of the following options represent the correct reduction of $XYZ + XYZ$?
 - a) 0
 - b) YZ
 - c) $X + X$
 - b) $2YZ$

- 5) What frequency division of the pulsed clock signal can be obtained by connecting 4 flip – flops in cascade?
 - a) 2
 - b) 4
 - c) 8
 - d) 16

Good Luck ☺