# Digital Logic Design (EL-1005) LABORATORY MANUAL Spring-2024



# LAB 07-B Binary Comparator

STUDENT NAME	ROLL NO	SEC			
	INSTRUCTOR SIGNATURE& DATE				
	MARKS AWARD	ED: /10			
NATIONAL UNIVERSITY OF COMPUTER AND EMERGING SCIENCES (NUCES), KARACHI					

# **Lab Session 07-B: Binary Comparator**

#### **OBJECTIVES**:

- > To learn and understand how to design a multiple output combinational circuit
- ➤ To learn and understand the working of 2-bit binary comparator
- To learn and understand the working and usage of Exclusive-OR and Exclusive-NOR gates

**APPARATUS:** Logic trainer, Logic probe

**COMPONENTS:** ICs 74LS08, 74LS32, 74LS04, 74LS86, 74LS02

#### **THEORY:**

Binary comparator is a combinational circuit that compares magnitude of two binary data signals A & B and generates the results of comparison in the form of three output signals A>B, A=B, A<B. Binary comparator is a multiple input and multiple output combinational circuit. When a combinational circuit has two or more than two outputs then each output is expressed separately as a function of all inputs. Separate K-map is made for each output.

#### One-bit comparator:

One-bit comparator compares magnitude of two numbers A and B, 1 bit each, and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 if A < B$$


$$E = 1 if A = B$$


$$G = 1 if A > B$$

#### **Truth Table:**

Inj	puts		Outputs	
A	В	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0


#### **K-Maps for Outputs:**

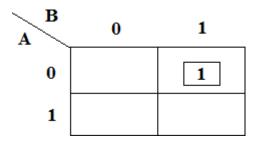

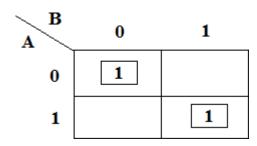

K-Map for Output L

K-Map for Output E

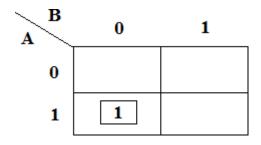

K-Map for Output G

# **Boolean Expressions of Outputs:**


L:  $\bar{A}B$ 

E:  $AB + \bar{A}\bar{B}_{\perp}$ 

**G:**  $A\bar{B}_{-}$ 
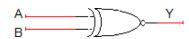
# **Exclusive-OR & Exclusive-NOR gates:**

The figure given below shows the symbol of Exclusive-OR (XOR) and Exclusive-NOR (XNOR) gates.






XNOR gate

XOR gate


Boolean expression of XNOR gate is

 $AB + \bar{A}\bar{B}$  and Boolean expression of XOR is  $\bar{A}B + A\bar{B}$ 

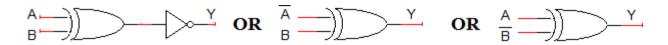. Boolean expression of XNOR gate can be implemented using XOR gate as shown in figure below:


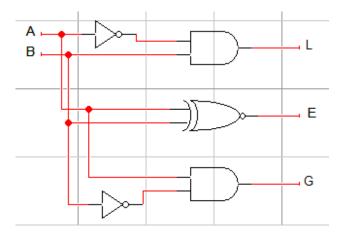
# Circuit Diagram for one-bit comparator:




In this experiment 74LS86 IC will be used for implementation of XOR gate function. 74LS86 IC contains four 2-input XOR gates. The function table and connection diagram for this IC are shown below:

# **Function Table:**

Inputs		Output	
A	В	Y	
L	L	L	
L	Н	H	
Н	L	H	
Н	Н	L	

H= Logic High, L= Logic Low

# **Connection Diagram:**

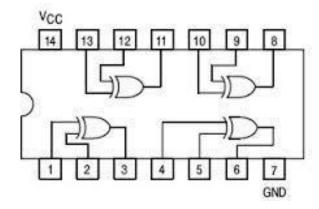



# **Lab Session 07-B Report Section BSE-2A**

Student\_ ID\_\_\_\_\_Date 4<sup>th</sup> March 2024

#### Lab Task #1

Design a combinational circuit that compares two 2-bit numbers and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 if A < B$$

$$E = 1 if A = B$$

$$G = 1 if A > B$$

# Lab Task #2

Design the combinational circuit of 2-Bit Binary comparator on Logic Works.

#### **INSTRUCTION FOR SUBMISSION**

Upload circuits of Task # 1 and Task # 2 on Google Classroom



**INSTRUCTOR: Muhammad Nadeem Ghouri**